


Transformer

An A.C. device used to change high voltage low current A.C. into low voltage high current A.C. and vice-versa without changing the frequency

In brief,

1. Transfers electric power from one circuit to another
2. It does so without a change of frequency
3. It accomplishes this by electromagnetic induction
4. Where the two electric circuits are in mutual inductive influence of each other.



Principle of operation

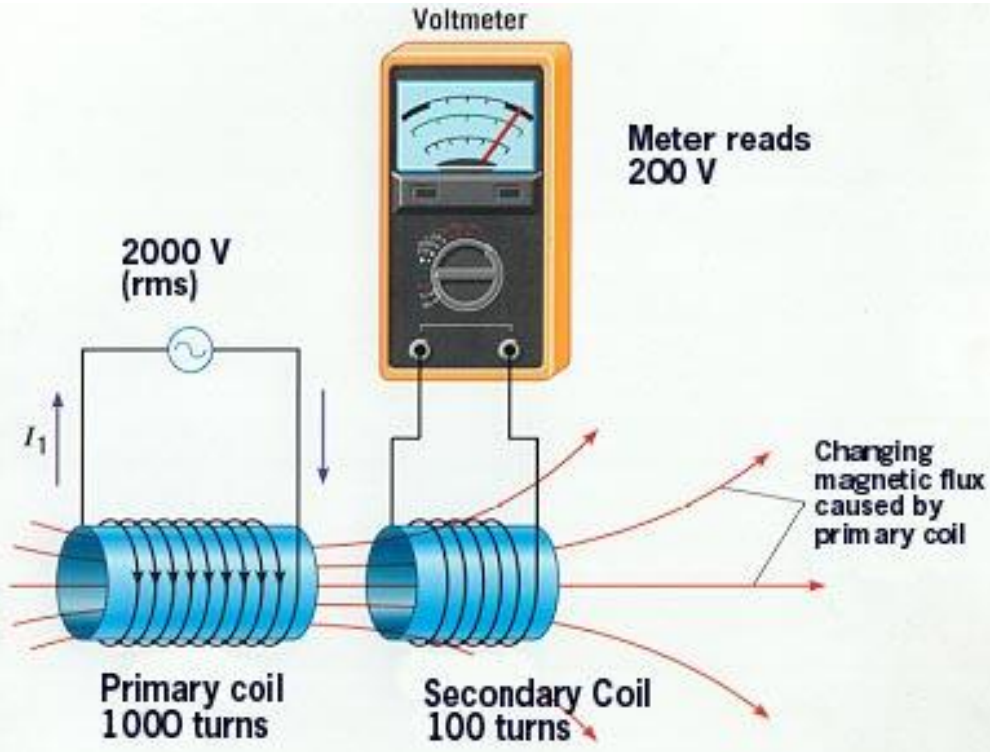

It is based on principle of **MUTUAL INDUCTION**.



According to which an e.m.f. is induced in a coil when current in the neighbouring coil changes.

Constructional detail : **Shell type**

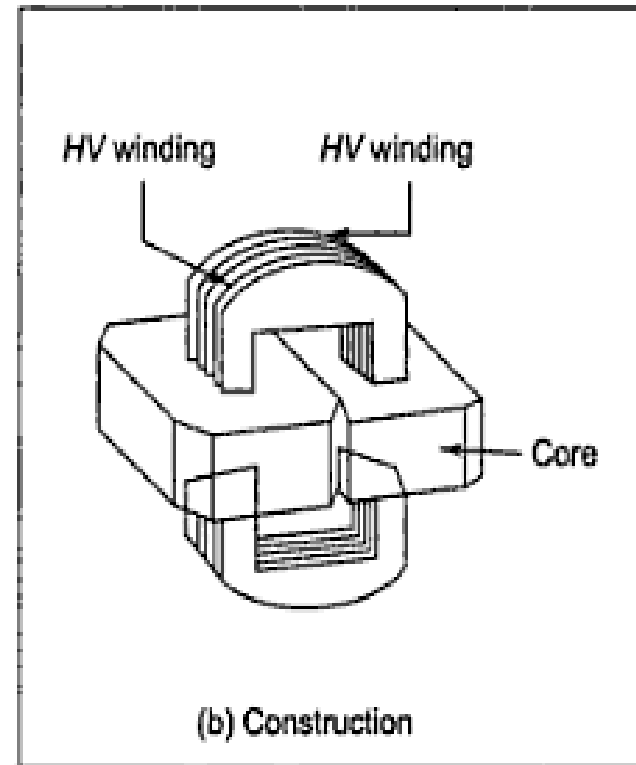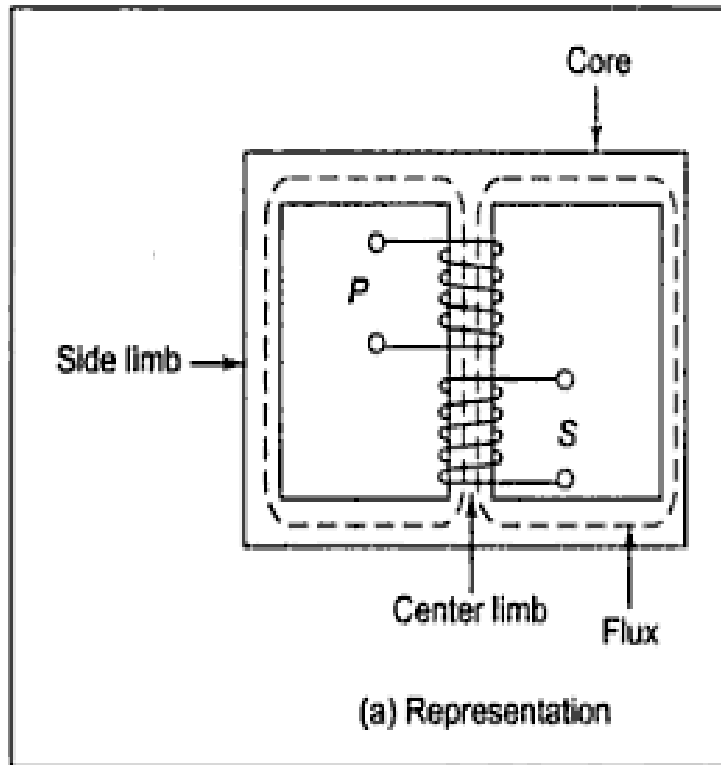


- Windings are wrapped around the center leg of a laminated core.

Core type

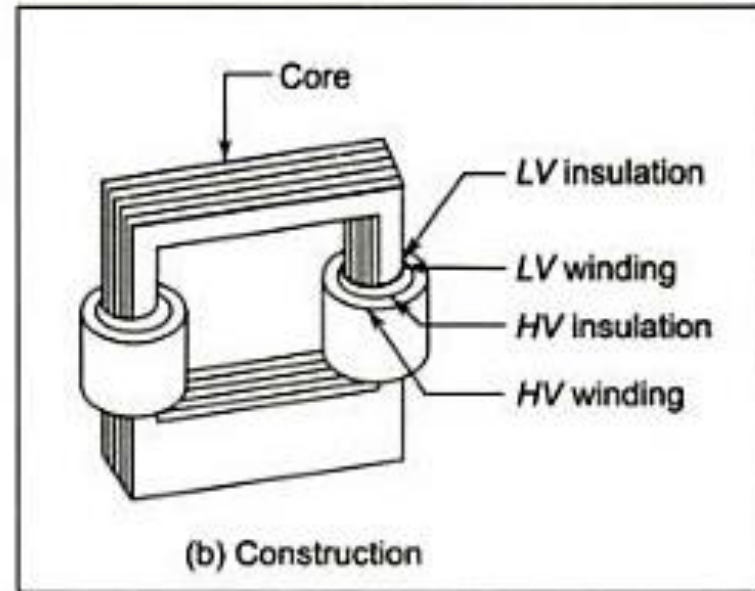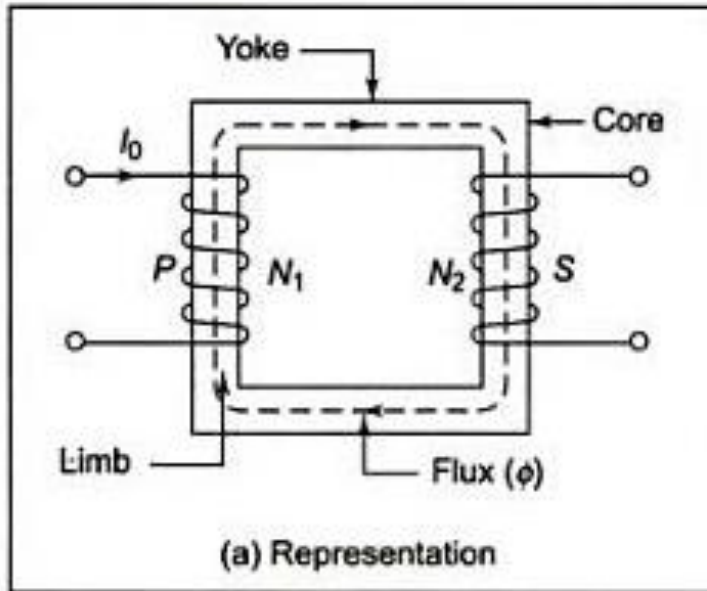

- Windings are wrapped around two sides of a laminated square core.

Sectional view of transformers

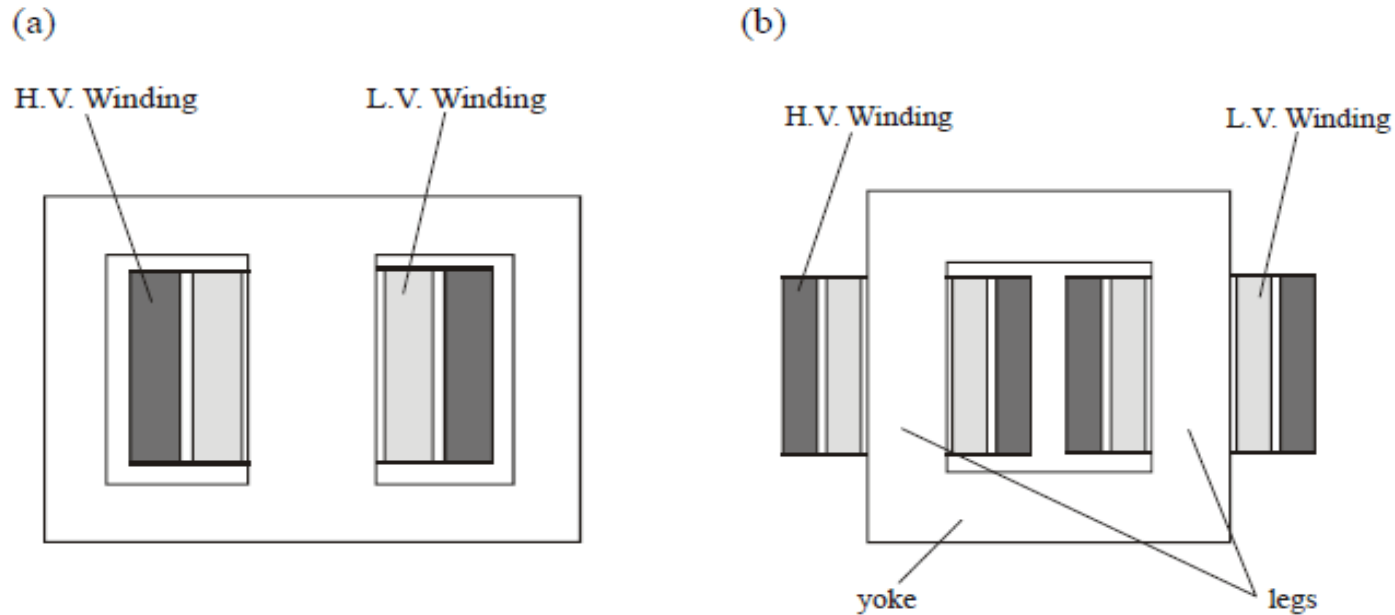


(a) Shell-type transformer, (b) core-type transformer

Note:


High voltage conductors are smaller cross section conductors than the low voltage coils

Construction of transformer from stampings

(a)

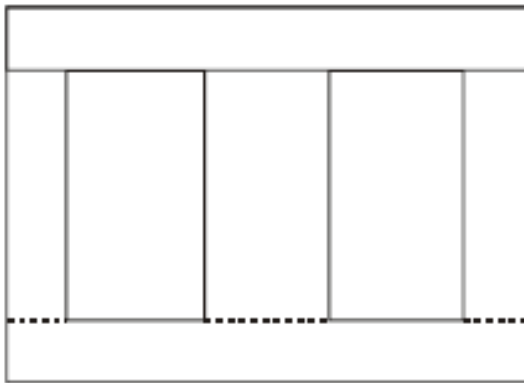

(b)

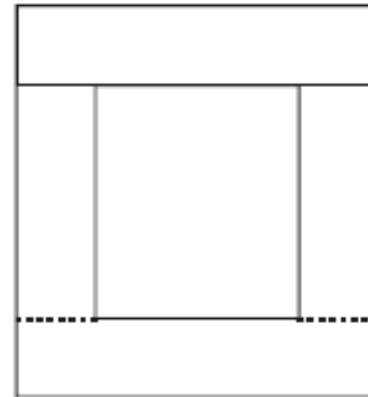

(a) Shell-type transformer, (b) core-type transformer

Core type

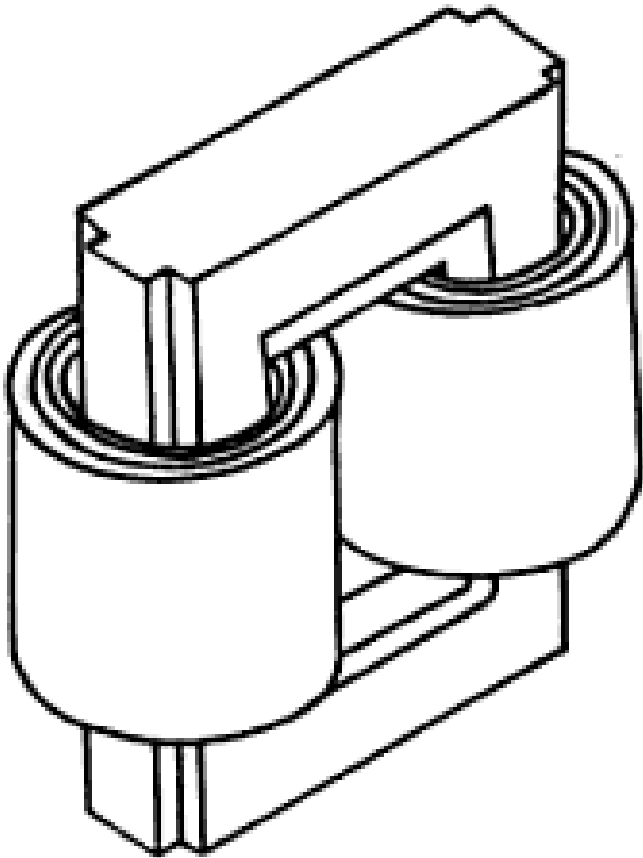


Fig1: Coil and laminations of core type transformer

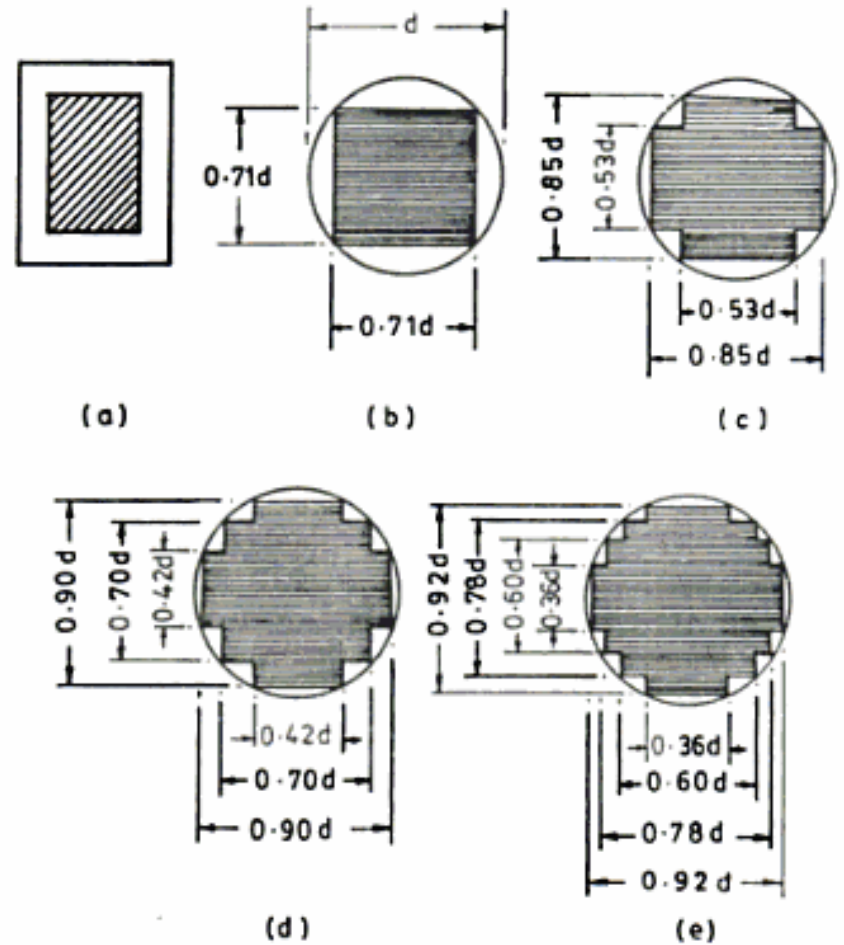


Fig2: Various types of cores

Shell type


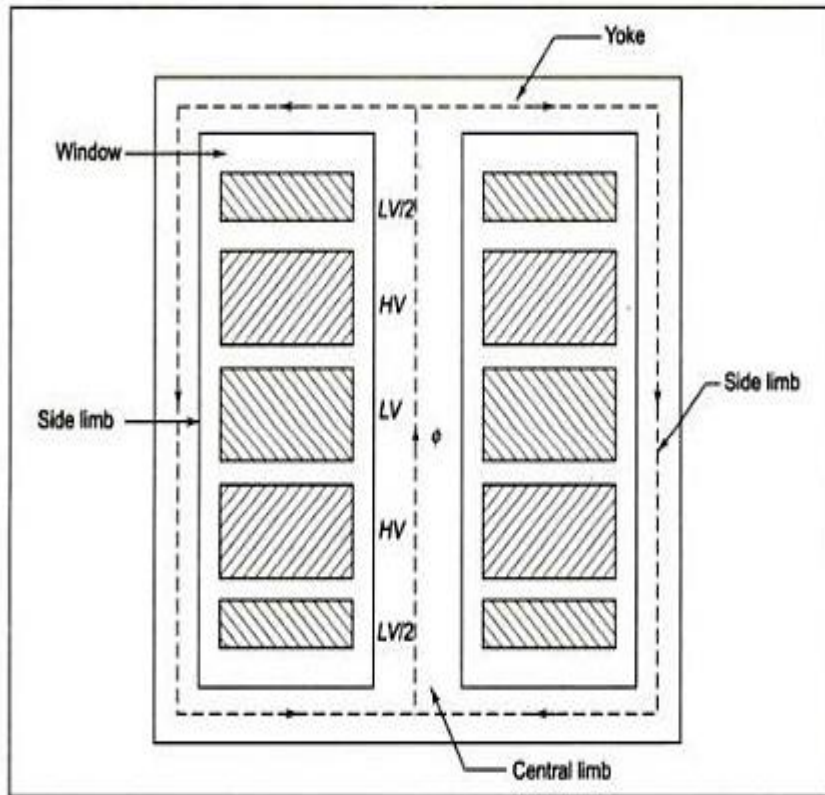



Fig: Sandwich windings

- The HV and LV windings are split into no. of sections
- Where HV winding lies between two LV windings
- In sandwich coils leakage can be controlled

Cut view of transformer

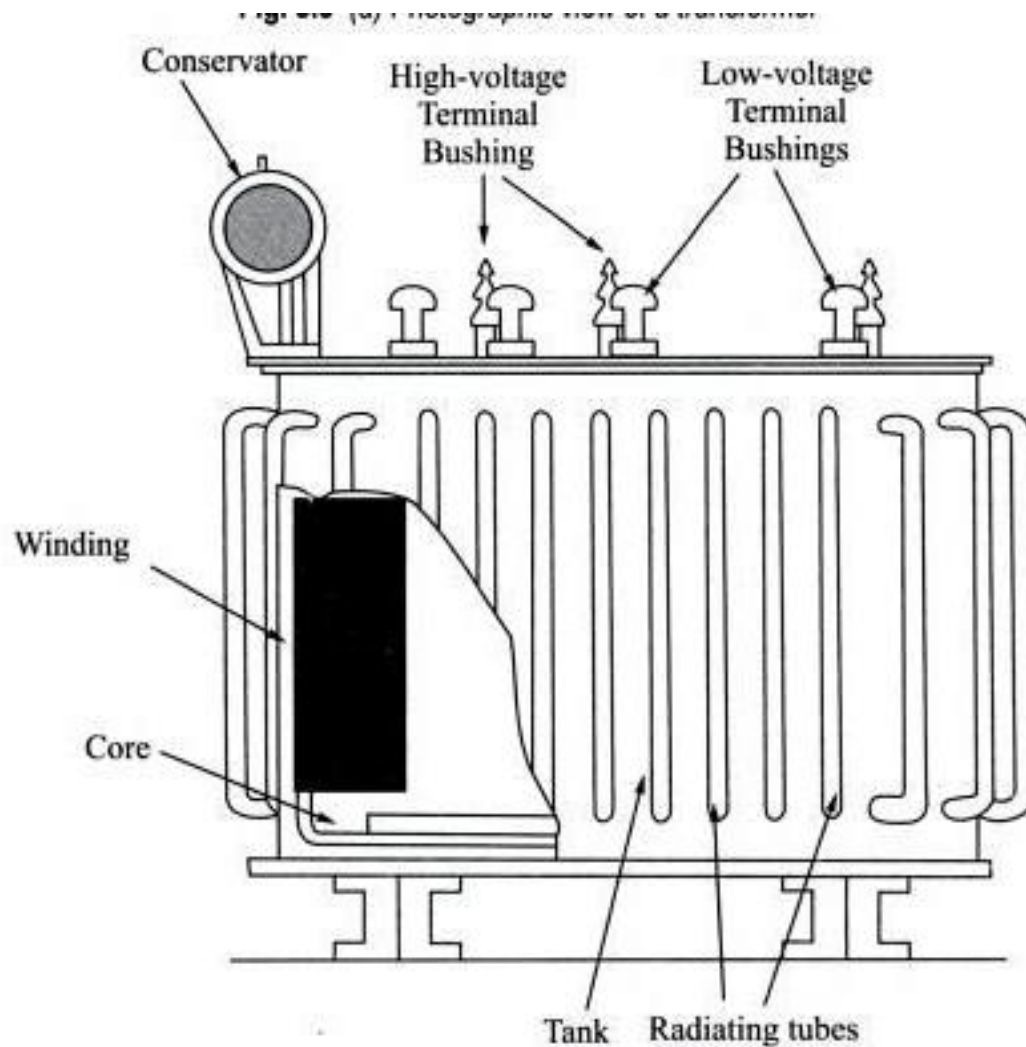


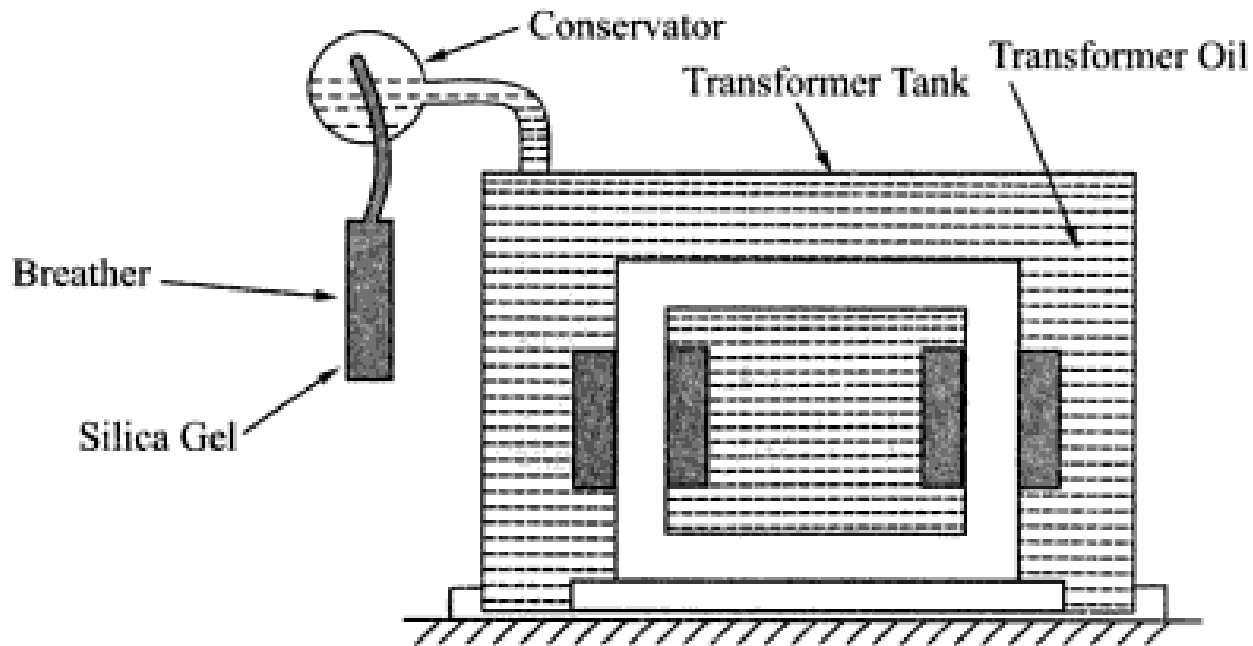Transformer with conservator and breather



Working of a transformer

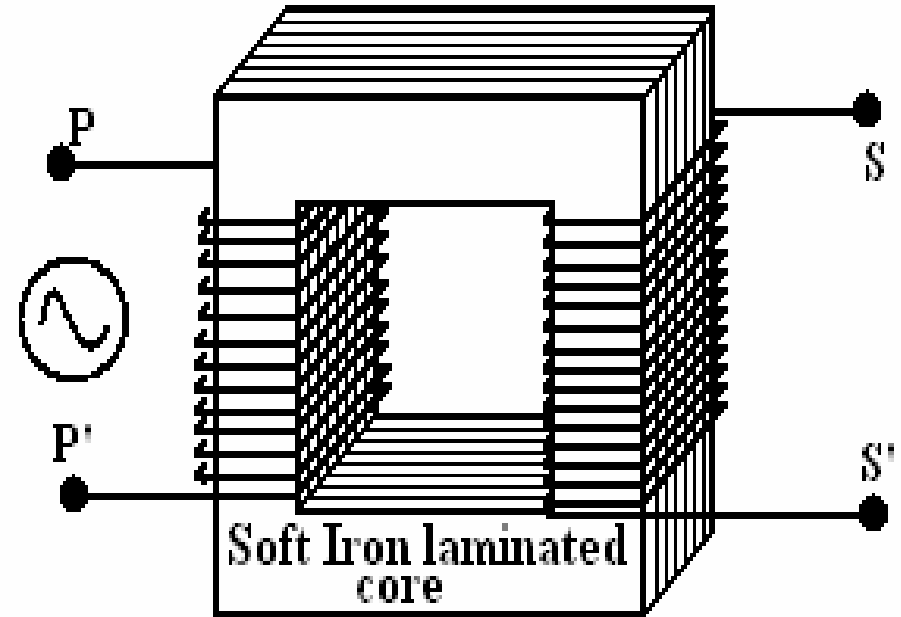1. When current in the primary coil changes being alternating in nature, a changing magnetic field is produced
2. This changing magnetic field gets associated with the secondary through the soft iron core
3. Hence magnetic flux linked with the secondary coil changes.
4. Which induces e.m.f. in the secondary.



Single Phase Transformer

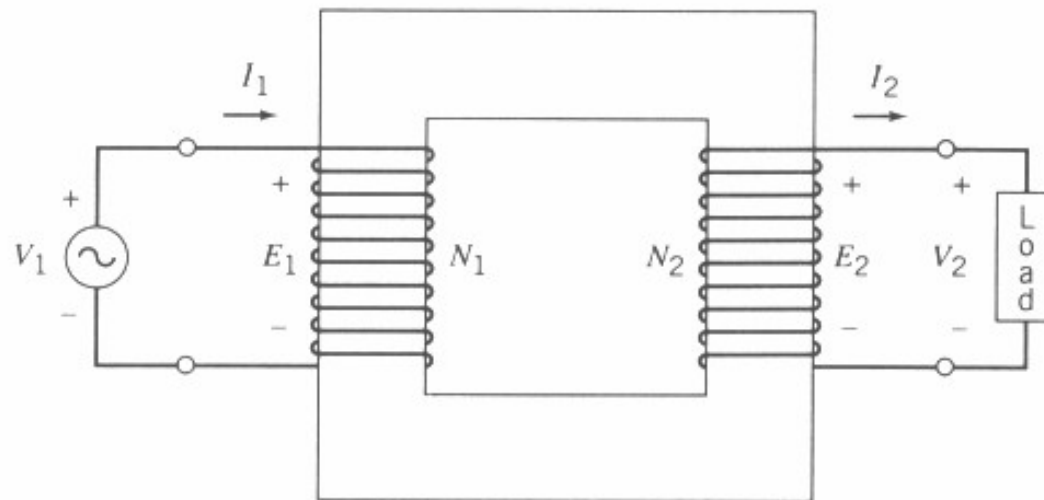




FIGURE 4.8 A transformer circuit.

- A single phase transformer
 - Two or more winding, coupled by a common magnetic core

Ideal Transformers

- **Zero leakage flux:**
 - Fluxes produced by the primary and secondary currents are confined within the core
- **The windings have no resistance:**
 - Induced voltages equal applied voltages
- **The core has infinite permeability**
 - Reluctance of the core is zero
 - Negligible current is required to establish magnetic flux
- **Loss-less magnetic core**
 - No hysteresis or eddy currents

Ideal transformer

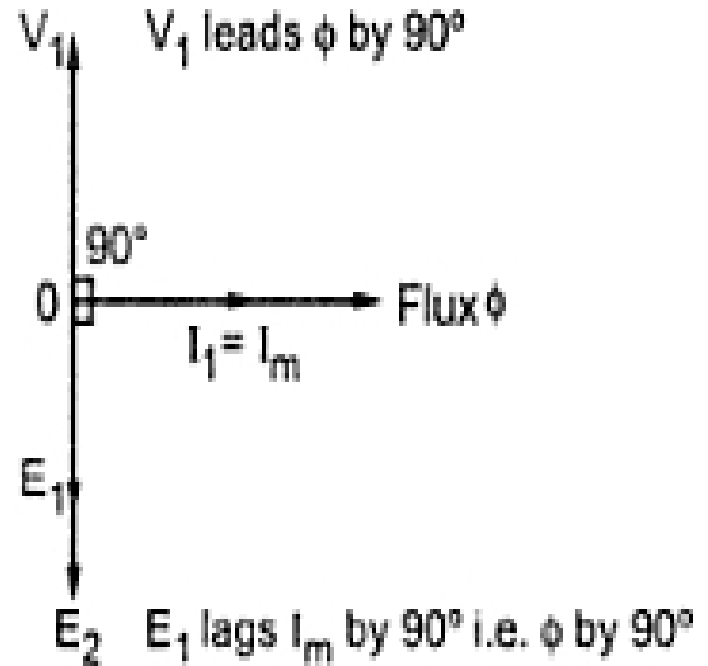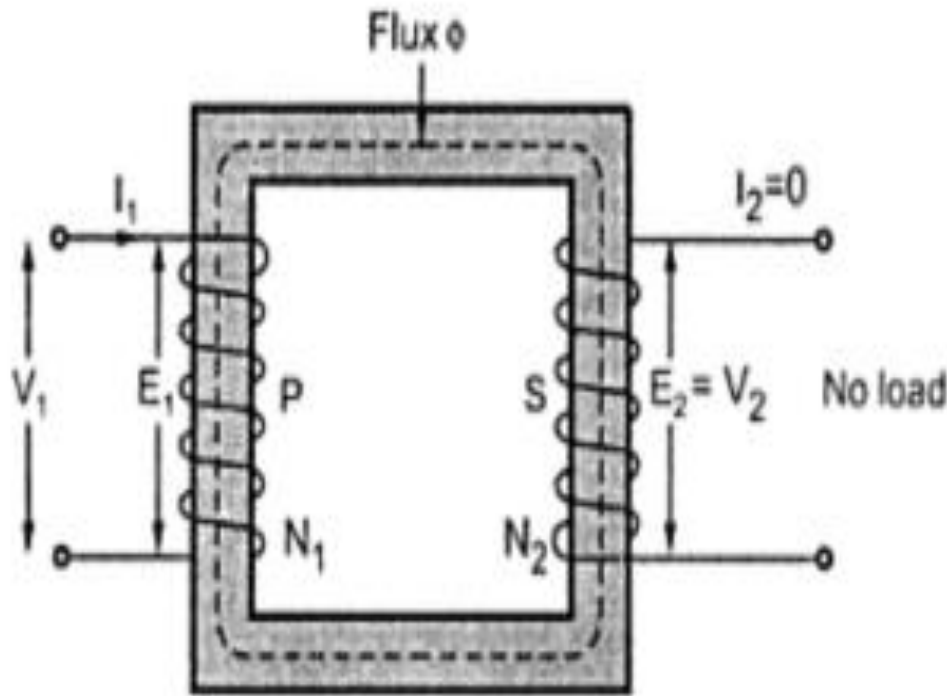


V_1 – supply voltage ;
 V_2 – output voltage;
 I_m – magnetising current;
 E_1 – self induced emf ;

I_1 – no load input current ;
 I_2 – output current
 E_2 – mutually induced emf

EMF equation of a transformer

- Worked out on board /
- [Refer pdf file: emf-equation-of-tranformer](#)

Phasor diagram: Transformer on No-load

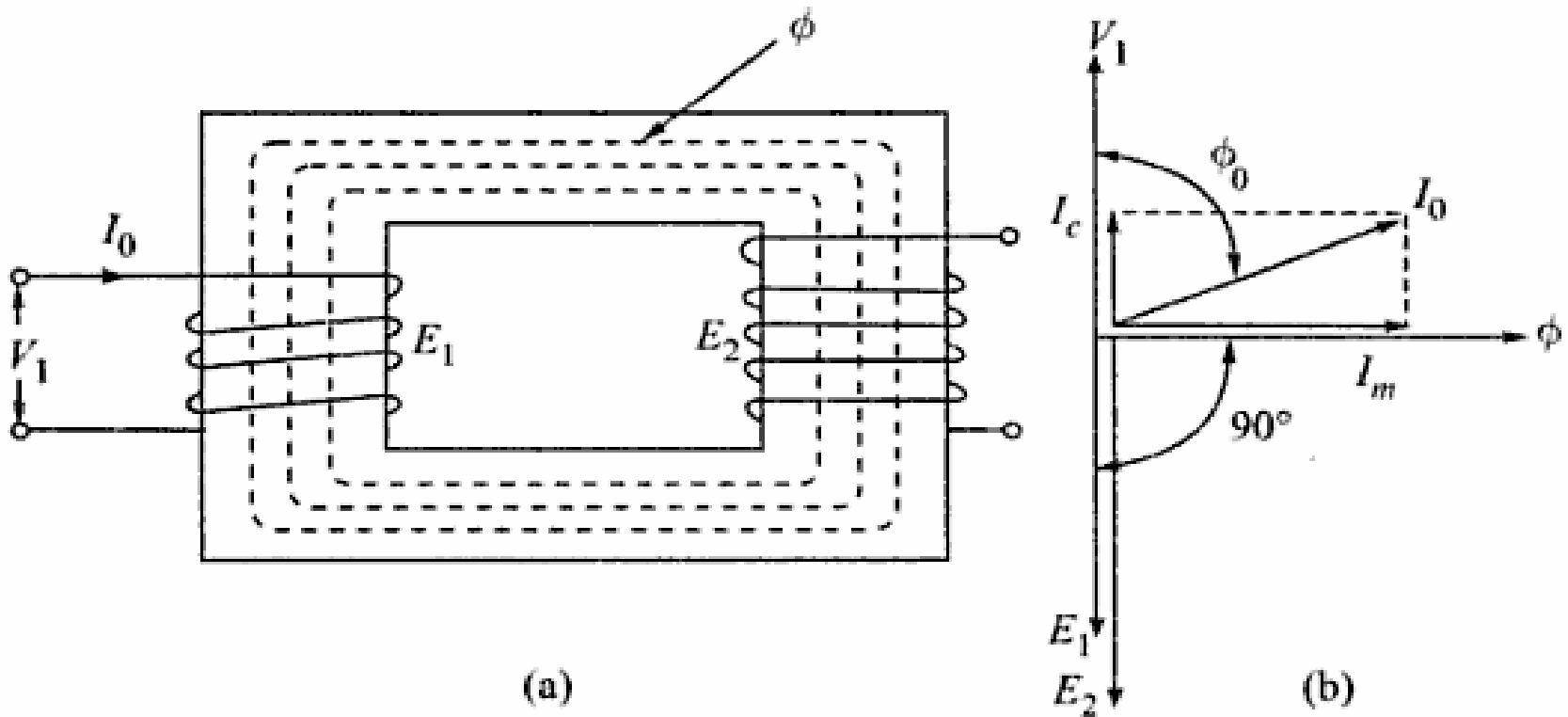

(a) Transformer on no-load (b) Phasor diagram of a transformer on no-load

Transformer on load assuming no voltage drop in the winding

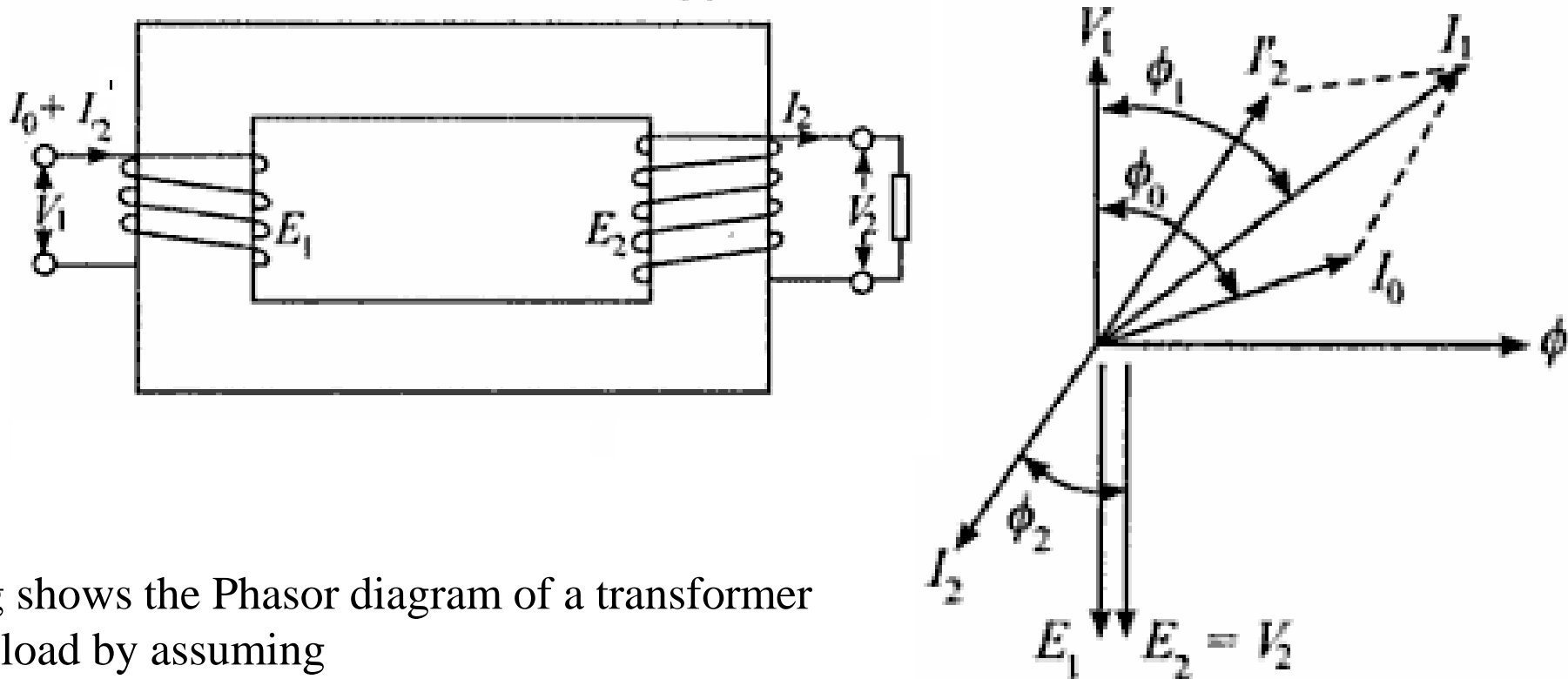


Fig shows the Phasor diagram of a transformer on load by assuming

1. No voltage drop in the winding
2. Equal no. of primary and secondary turns

Transformer on load

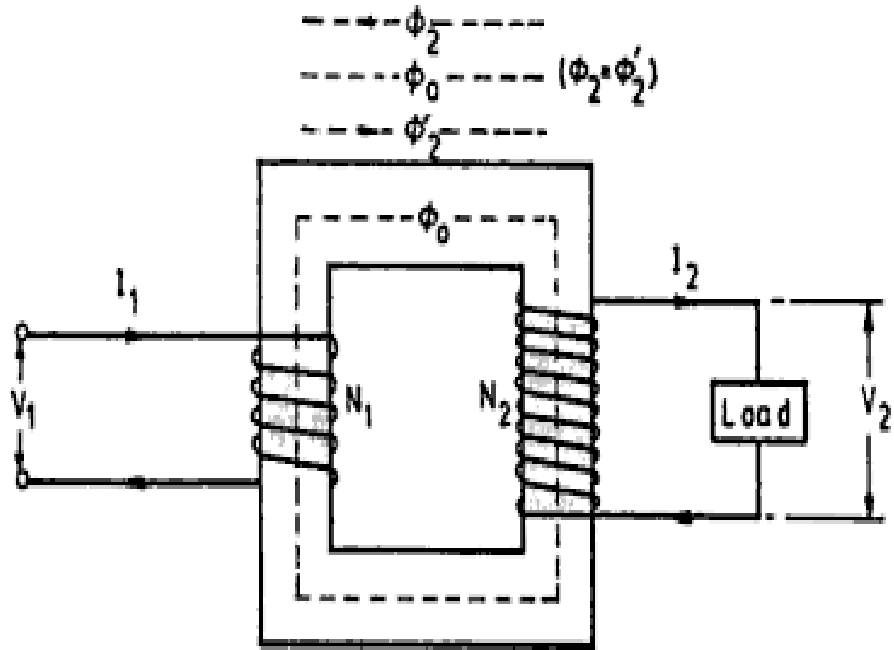


Fig. a: Ideal transformer on load



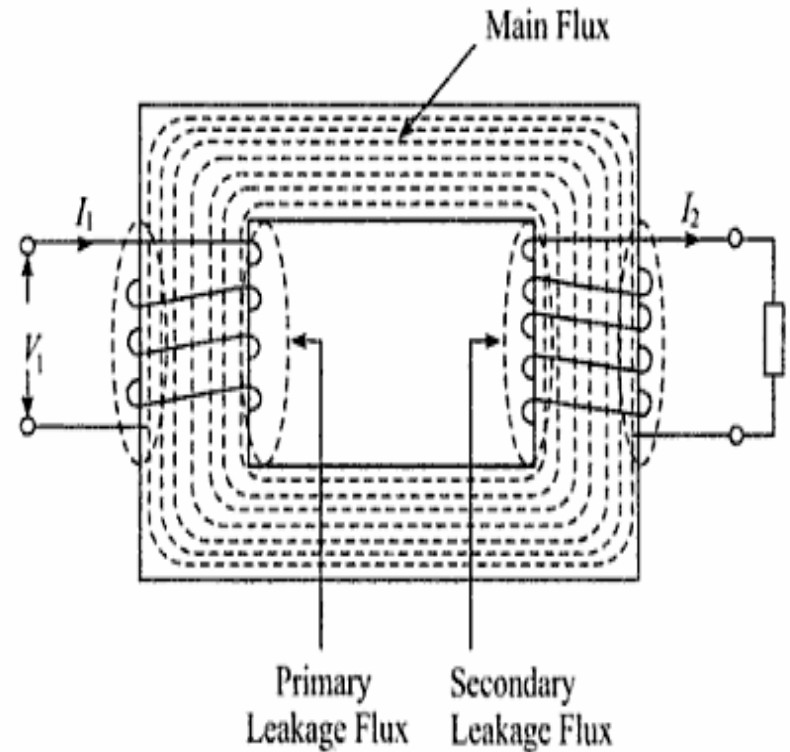


Fig. b: Main flux and leakage flux in a transformer

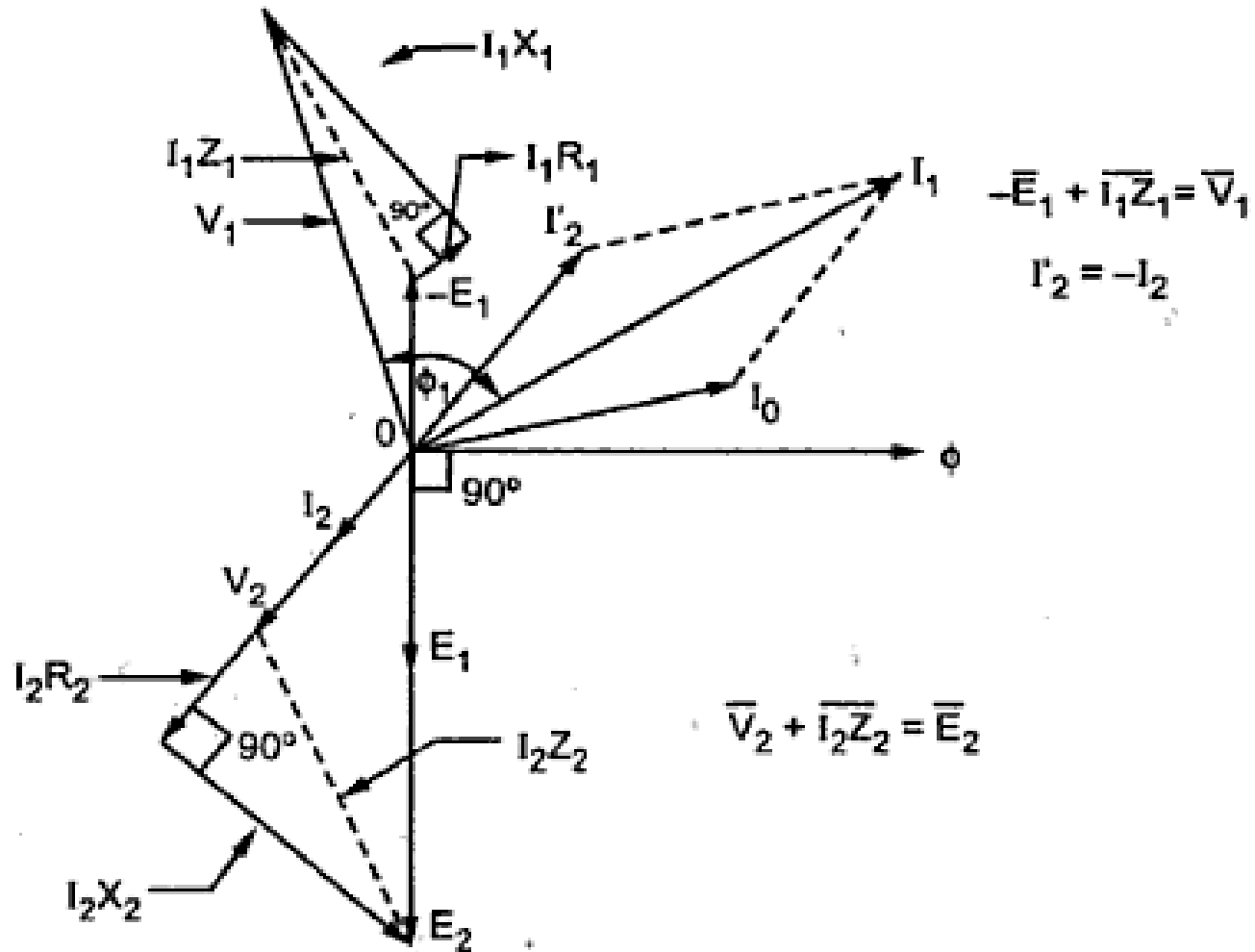
Phasor diagram of transformer with UPF load



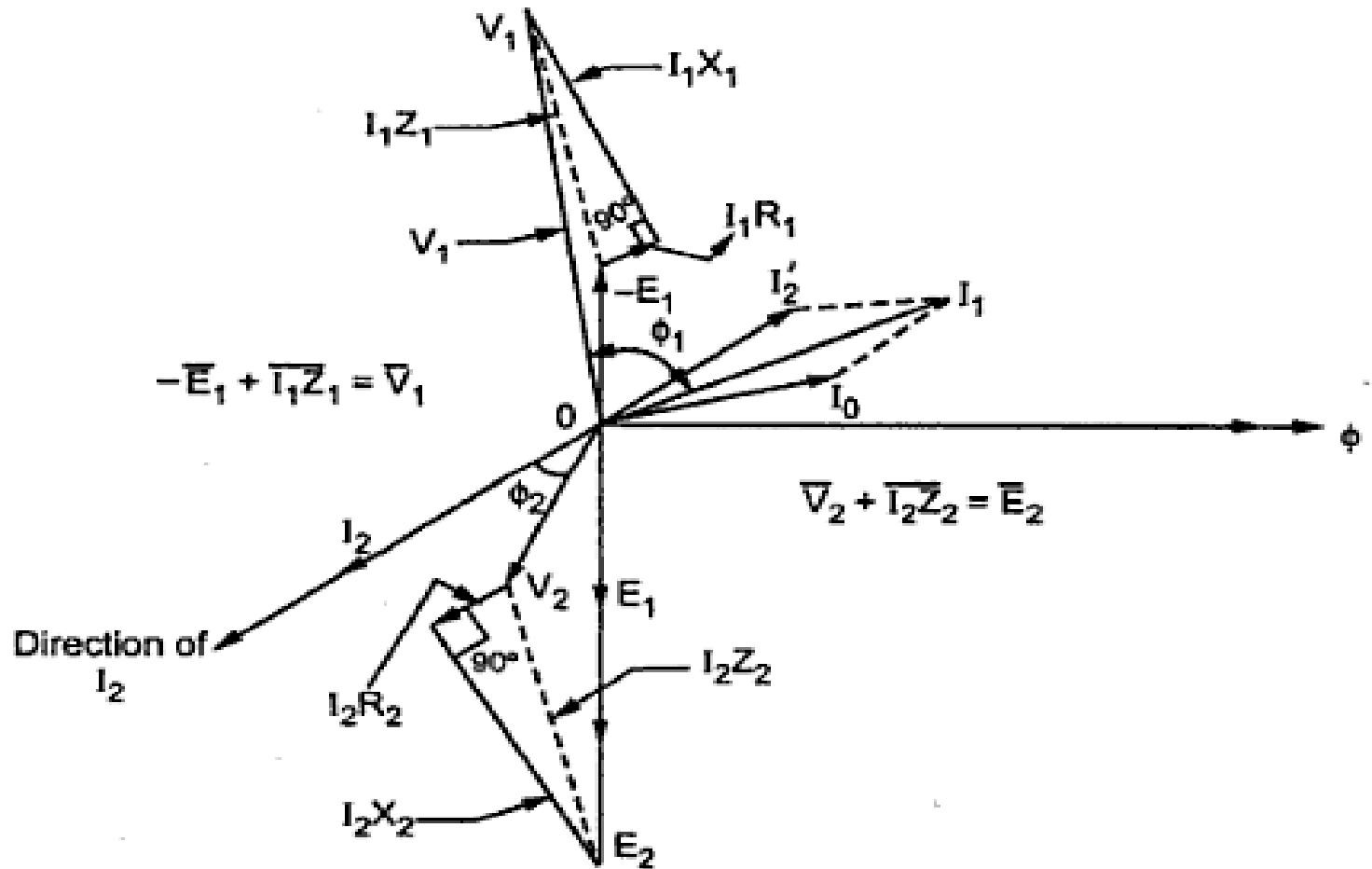Phasor diagram of transformer with lagging p.f load




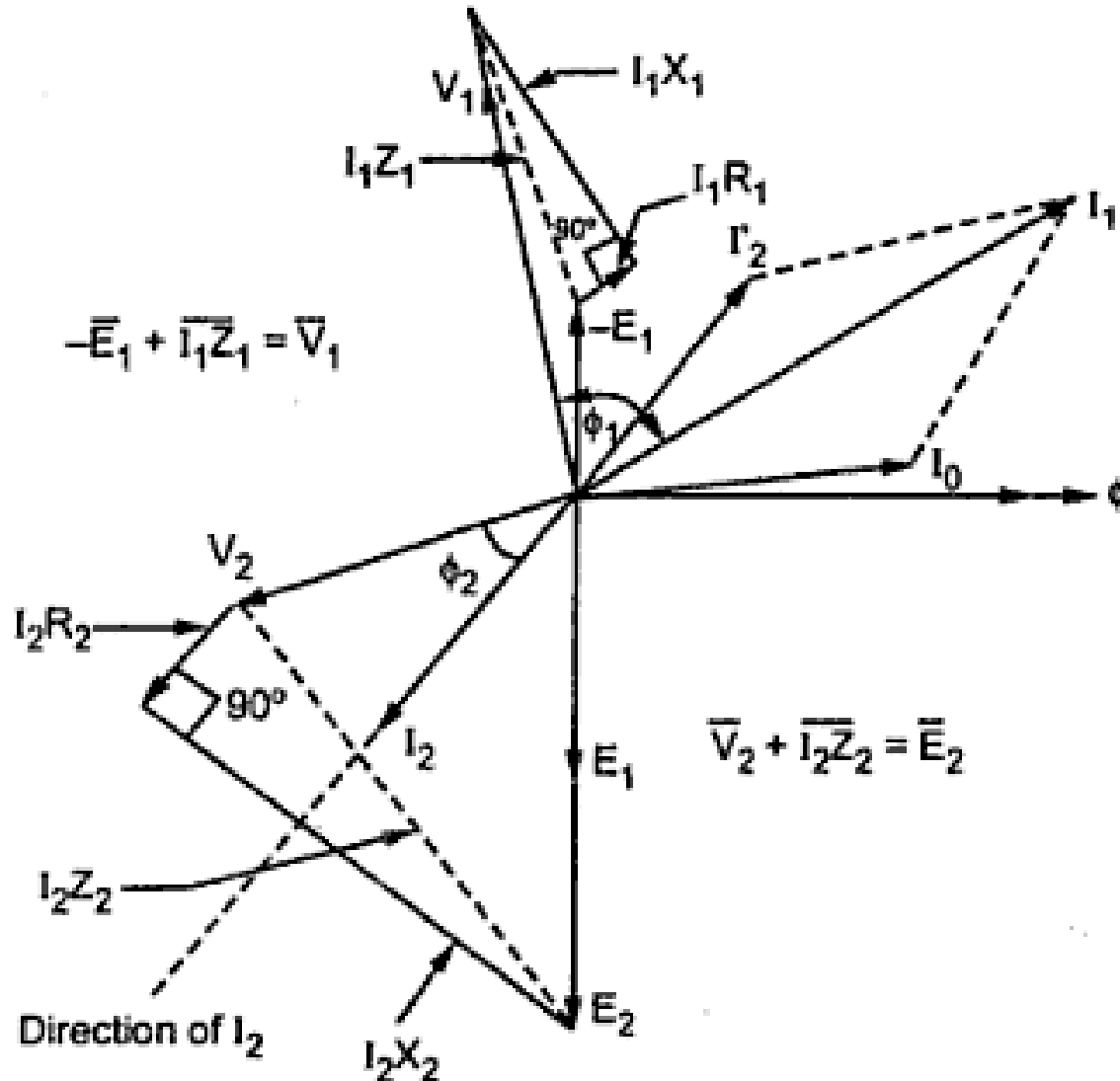Phasor diagram of transformer with leading p.f load



Equivalent circuit of a transformer

No load equivalent circuit:

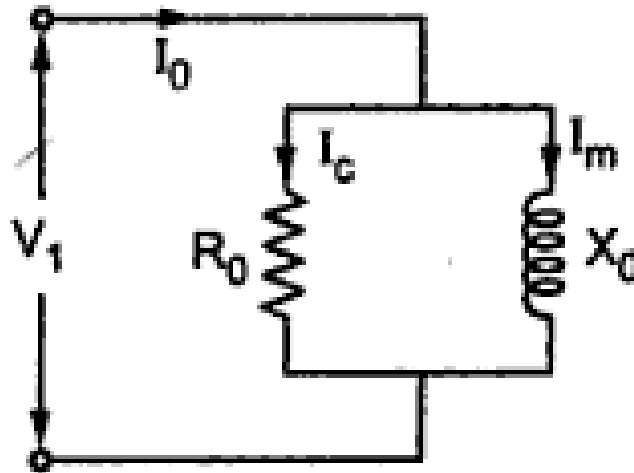



$$R_0 = \frac{V_1}{I_c}$$

$$X_0 = \frac{V_1}{I_m}$$

$$I_m = I_0 \sin \phi_0 = \text{Magnetising component}$$

$$I_c = I_0 \cos \phi_0 = \text{Active component}$$

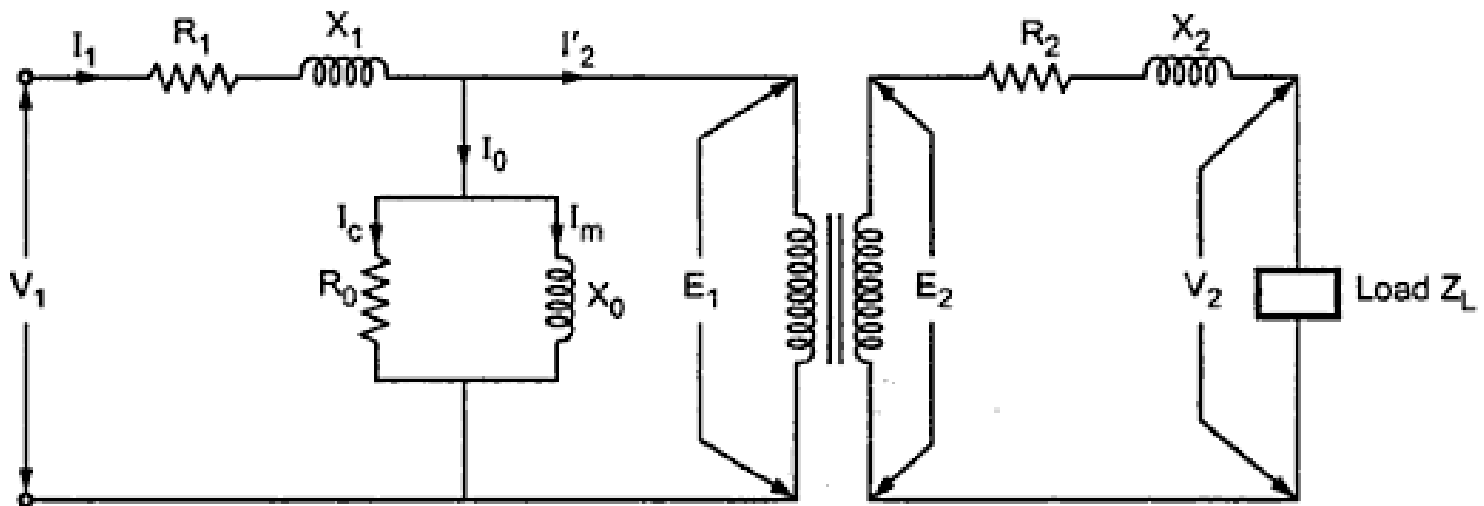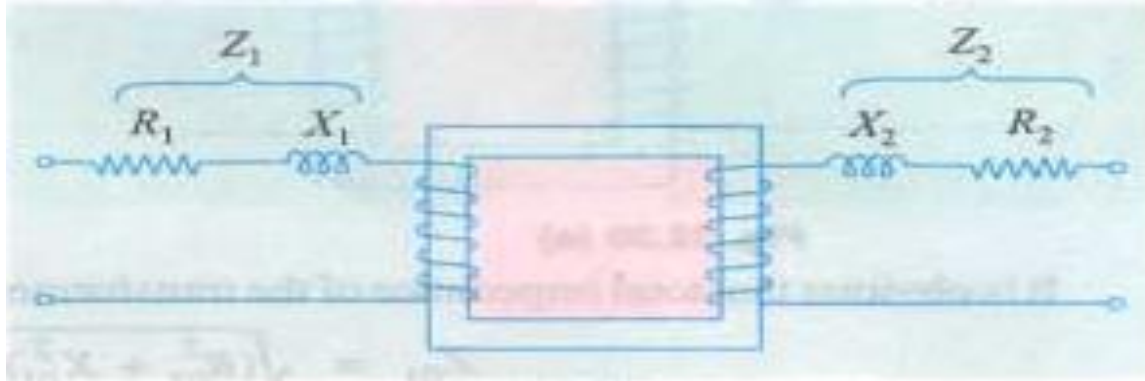Equivalent circuit parameters referred to primary and secondary sides respectively



Contd.,

- The effect of circuit parameters shouldn't be changed while transferring the parameters from one side to another side
- It can be proved that a resistance of R_2 in sec. is equivalent to R_2/k^2 will be denoted as R_2' (ie. Equivalent sec. resistance w.r.t primary) which would have caused the same loss as R_2 in secondary,


$$\begin{aligned} I_1^2 R_2' &= I_2^2 R_2 \\ R_2' &= \left(\frac{I_2}{I_1} \right)^2 R_2 \\ &= \frac{R_2}{k^2} \end{aligned}$$

Transferring secondary parameters to primary side

$$R'_2 = \frac{R_2}{K^2}, \quad X'_2 = \frac{X_2}{K^2}, \quad Z'_2 = \frac{Z_2}{K^2}$$

While $E'_2 = \frac{E_2}{K}, \quad I'_2 = KI_2$

where $K = \frac{N_2}{N_1}$

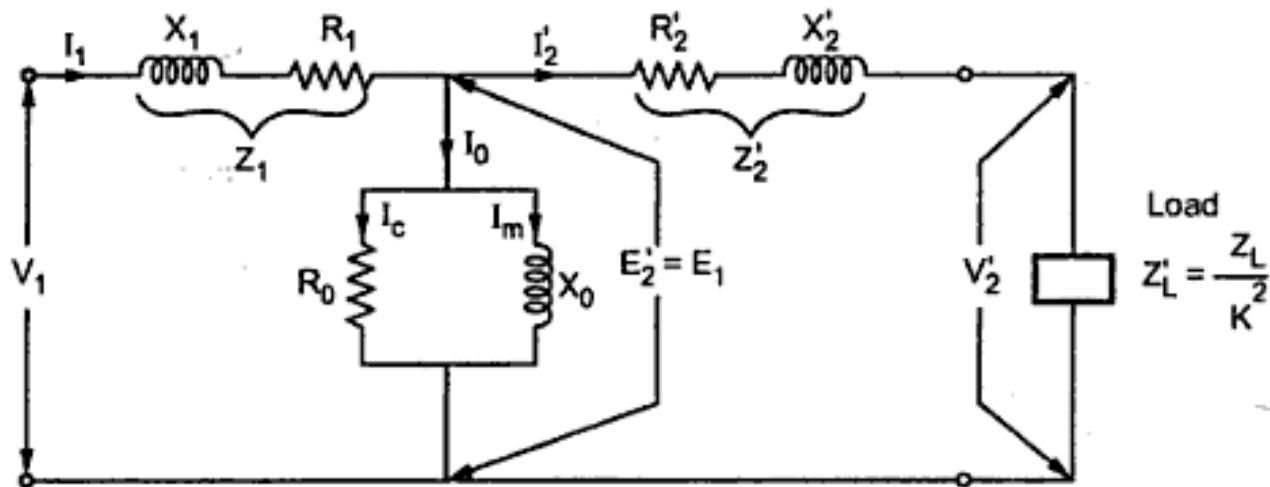

Exact equivalent circuit referred to primary


Equivalent circuit referred to secondary side

- Transferring primary side parameters to secondary side



$$R'_1 = K^2 R_1, \quad X'_1 = K^2 X_1, \quad Z'_1 = K^2 Z_1$$

$$E'_1 = K E_1, \quad I'_1 = \frac{I_1}{K}, \quad I'_0 = \frac{I_0}{K}$$

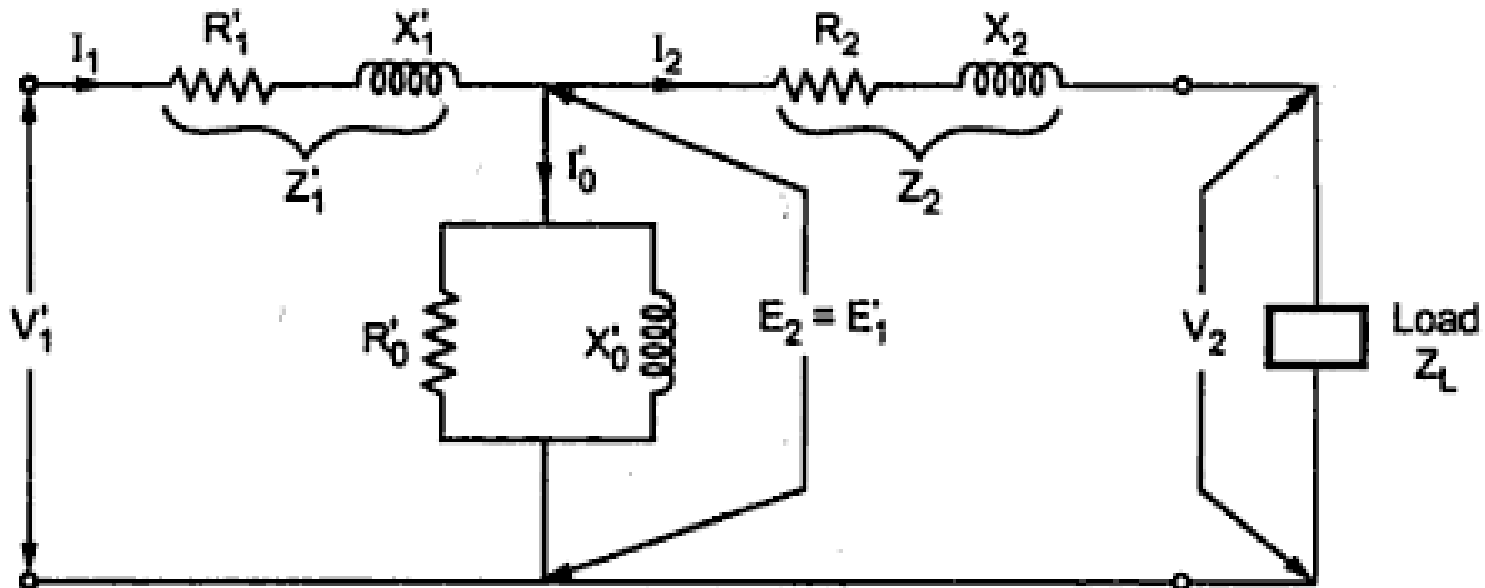Similarly exciting circuit parameters are also transferred to secondary as R_o' and X_o'



equivalent circuit w.r.t primary

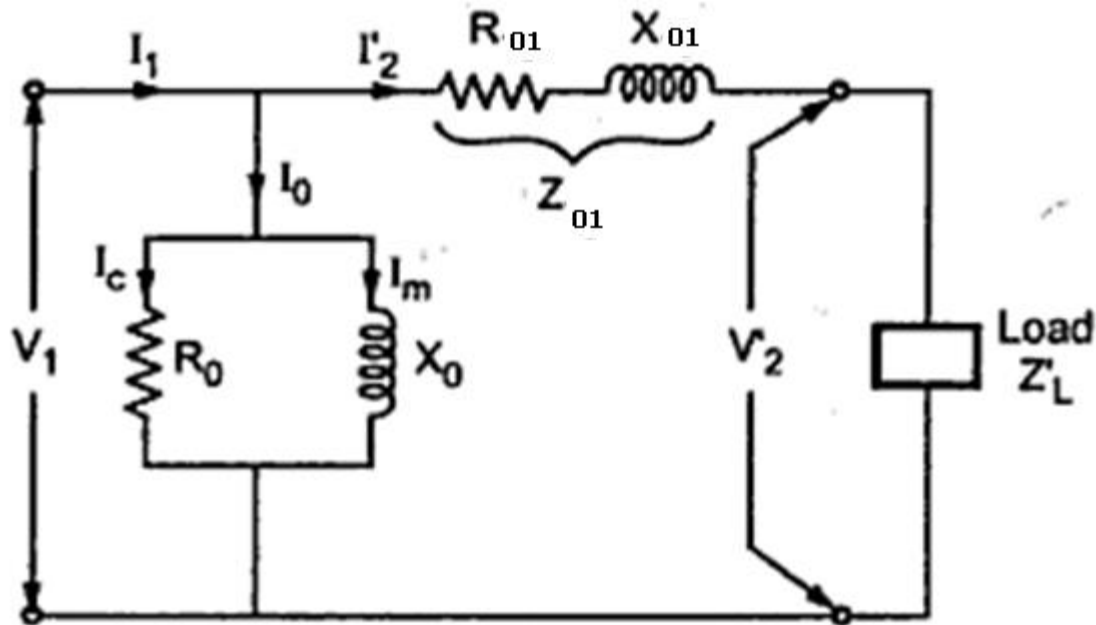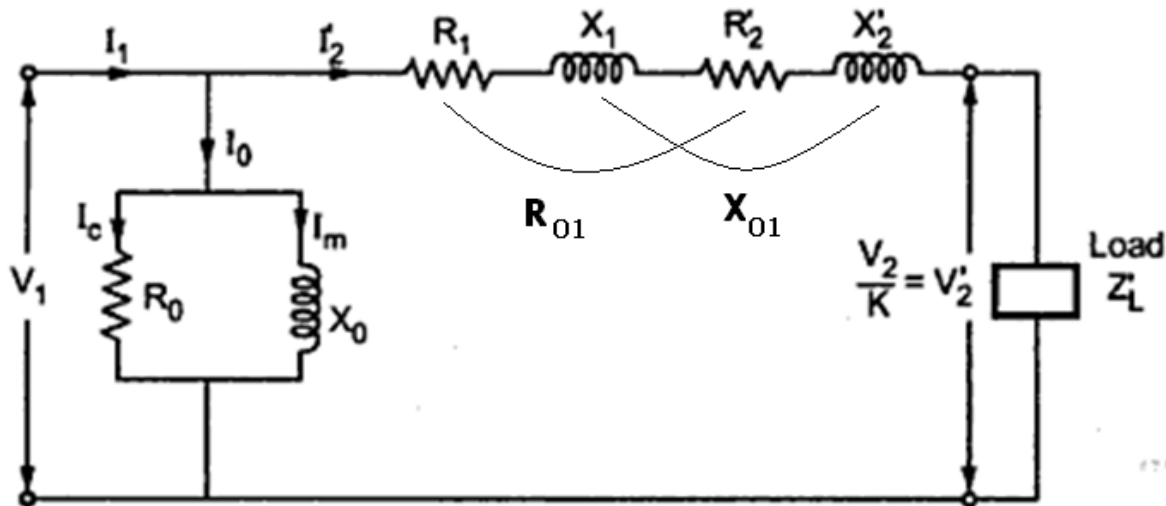

where


$$R_{01} = R_1 + R'_2 = R_1 + \frac{R_2}{K^2}$$

$$X_{01} = X_1 + X'_2 = X_1 + \frac{X_2}{K^2}$$

$$Z_{01} = R_{01} + j X_{01}$$

Approximate equivalent circuit

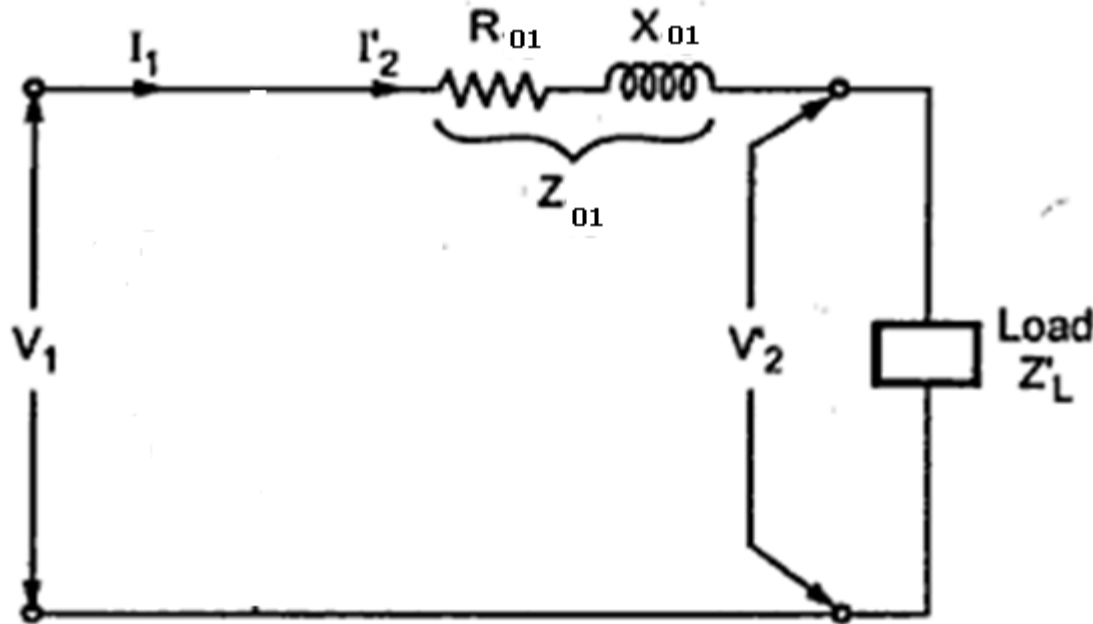- Since the no-load current is 1% of the full load current, the no-load circuit can be neglected




Transformer Tests

- The performance of a transformer can be calculated on the basis of equivalent circuit
- The four main parameters of equivalent circuit are:
 - R_{01} as referred to primary (or secondary R_{02})
 - the equivalent leakage reactance X_{01} as referred to primary (or secondary X_{02})
 - Magnetising susceptance B_0 (or reactance X_0)
 - core loss conductance G_0 (or resistance R_0)
- The above constants can be easily determined by two tests
 - Open circuit test (O.C test / No load test)
 - Short circuit test (S.C test/Impedance test)
- These tests are economical and convenient
 - these tests furnish the result without actually loading the transformer

Open-circuit Test

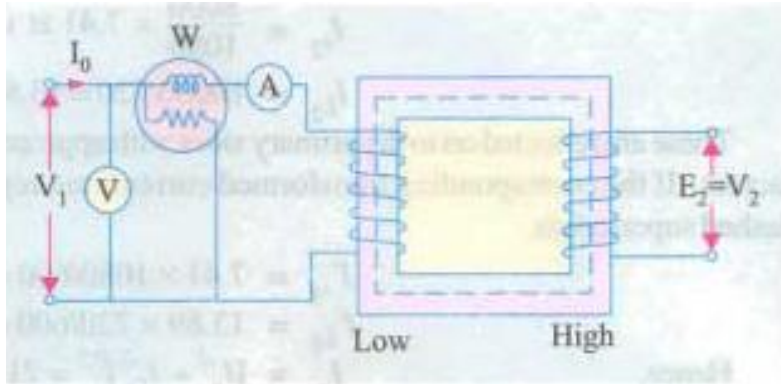In Open Circuit Test the transformer's *secondary winding is open-circuited*, and its *primary winding is connected to a full-rated line voltage*.



$$\text{Core loss} = W_{oc} = V_0 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{W_{oc}}{V_0 I_0}$$

$$I_c \text{ or } I_w = I_0 \cos \phi_0$$

$$I_m \text{ or } I_\mu = I_0 \sin \phi_0 = \sqrt{I_0^2 - I_w^2}$$

$$I_0 = V_0 Y_0; \quad \therefore Y_0 = \frac{I_0}{V_0}$$

$$R_0 = \frac{V_0}{I_w}$$

$$X_0 = \frac{V_0}{I_\mu}$$

$$G_0 = \frac{I_w}{V_0}$$

$$B_0 = \frac{I_\mu}{V_0}$$

$$W_{oc} = V_0^2 G_0; \quad \therefore \text{Exciting conductance } G_0 = \frac{W_{oc}}{V_0^2}$$


$$\& \text{ Exciting susceptance } B_0 = \sqrt{Y_0^2 - G_0^2}$$

- Usually conducted on H.V side
- To find
 - (i) No load loss or core loss
 - (ii) No load current I_0 which is helpful in finding G_0 (or R_0) and B_0 (or X_0)

Short-circuit Test


In Short Circuit Test the *secondary terminals are short circuited*, and the *primary terminals are connected to a fairly low-voltage source*

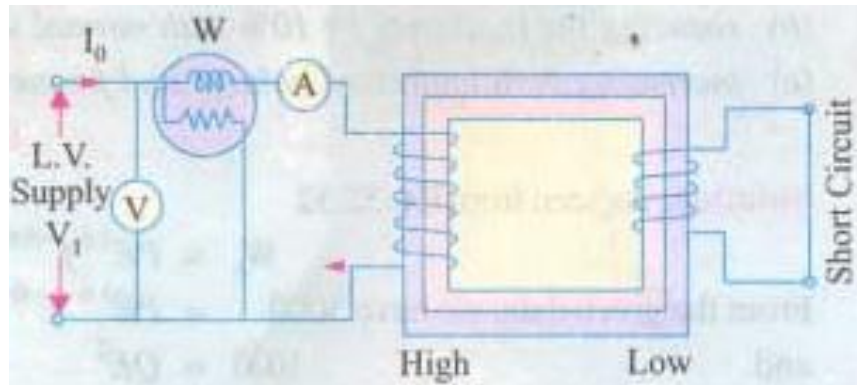The input voltage is adjusted until the current in the short circuited windings is equal to its rated value. The input voltage, current and power is measured.



- Usually conducted on L.V side
- To find
 - (i) Full load copper loss – to pre determine the efficiency
 - (ii) Z_{01} or Z_{02} ; X_{01} or X_{02} ; R_{01} or R_{02} - to predetermine the voltage regulation

Contd...

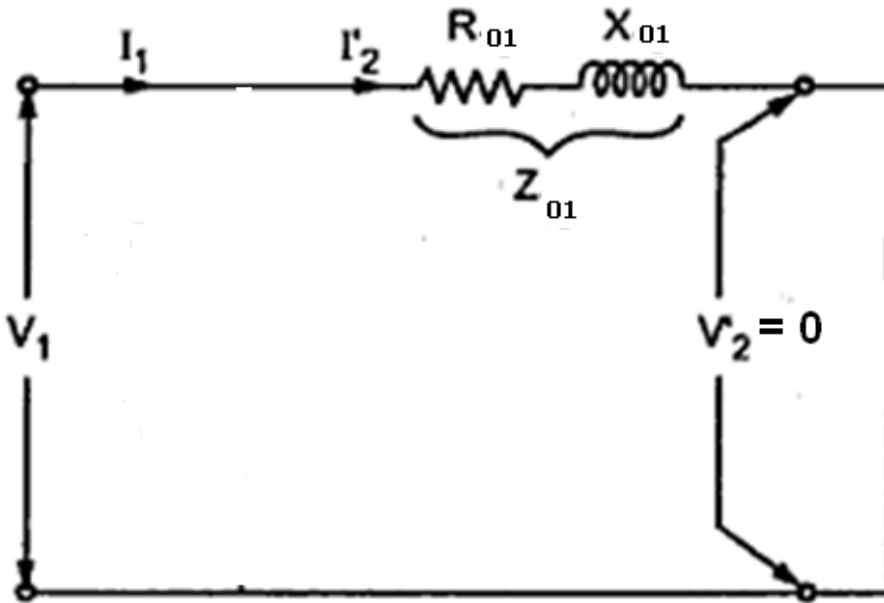

$$\text{Full load cu loss} = W_{sc} = I_{sc}^2 R_{01}$$

$$R_{01} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{01} = \frac{V_{sc}}{I_{sc}}$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

Transformer Voltage Regulation and Efficiency

The output voltage of a transformer varies with the load even if the input voltage remains constant. This is because a real transformer has series impedance within it. Full load Voltage Regulation is a quantity that compares the output voltage at no load with the output voltage at full load, defined by this equation:

$$\text{Regulation up} = \frac{V_{S,nl} - V_{S,fl}}{V_{S,fl}} \times 100\%$$

$$\text{Regulation down} = \frac{V_{S,nl} - V_{S,fl}}{V_{S,nl}} \times 100\%$$

$$\text{At no load } k = \frac{V_s}{V_p}$$

$$\text{Regulation up} = \frac{(V_P / k) - V_{S,fl}}{V_{S,fl}} \times 100\%$$

$$\text{Regulation down} = \frac{(V_P / k) - V_{S,fl}}{V_{S,nl}} \times 100\%$$

Ideal transformer, VR = 0%.

Voltage regulation of a transformer

$$\text{Voltage regulation} = \frac{\text{no - load voltage} - \text{full - load voltage}}{\text{no - load voltage}}$$

recall $\frac{V_s}{V_p} = \frac{N_s}{N_p}$

Secondary voltage on no-load $V_2 = V_1 \left(\frac{N_2}{N_1} \right)$


V_2 is a secondary terminal voltage on full load

Substitute we have

$$\text{Voltage regulation} = \frac{V_1 \left(\frac{N_2}{N_1} \right) - V_2}{V_1 \left(\frac{N_2}{N_1} \right)}$$

Transformer Phasor Diagram

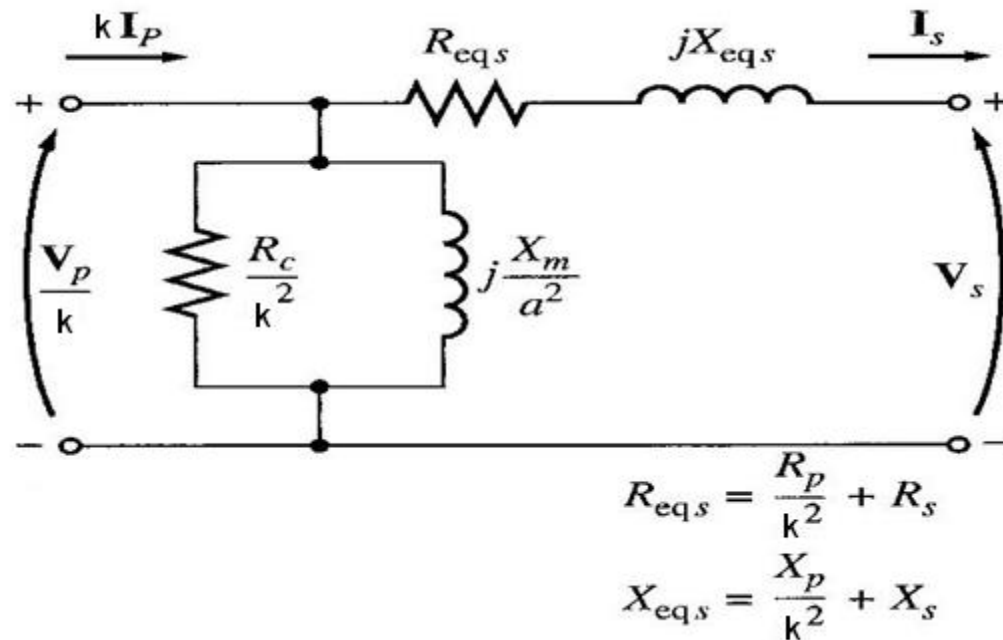To determine the voltage regulation of a transformer, it is necessary understand the voltage drops within it.



Transformer Phasor Diagram

Ignoring the excitation of the branch (since the current flow through the branch is considered to be small), more consideration is given to the series impedances ($R_{eq} + jX_{eq}$).

Voltage Regulation depends on magnitude of the series impedance and the phase angle of the current flowing through the transformer.

Phasor diagrams will determine the effects of these factors on the voltage regulation. A phasor diagram consist of current and voltage vectors.


Assume that the reference phasor is the secondary voltage, V_S . Therefore the reference phasor will have 0 degrees in terms of angle.

Based upon the equivalent circuit, apply Kirchoff Voltage Law,


$$\frac{V_P}{k} = V_S + R_{eq} I_S + jX_{eq} I_S$$

Transformer Phasor Diagram

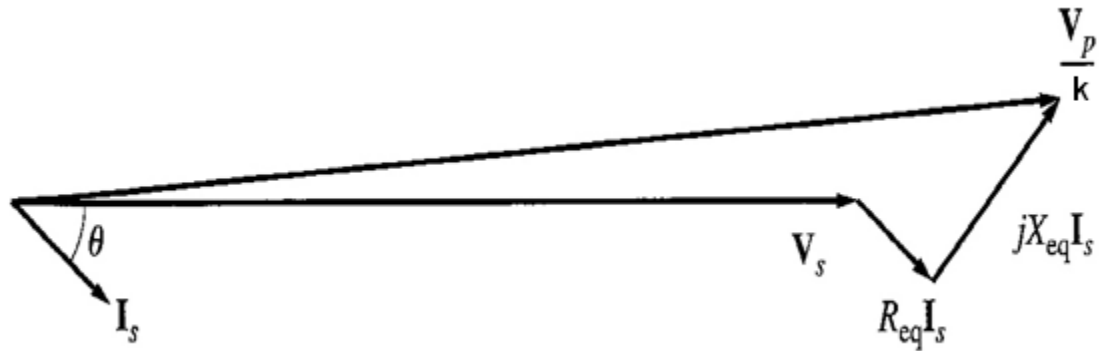For lagging loads, $V_p / a > V_c$ so the voltage regulation with lagging loads is > 0 .




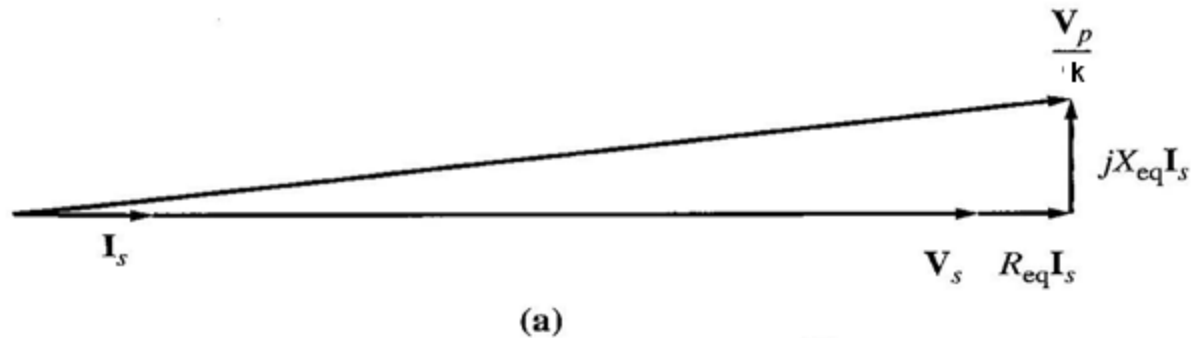When the power factor is unity, V_s is lower than V_p so $VR > 0$.




Transformer Phasor Diagram

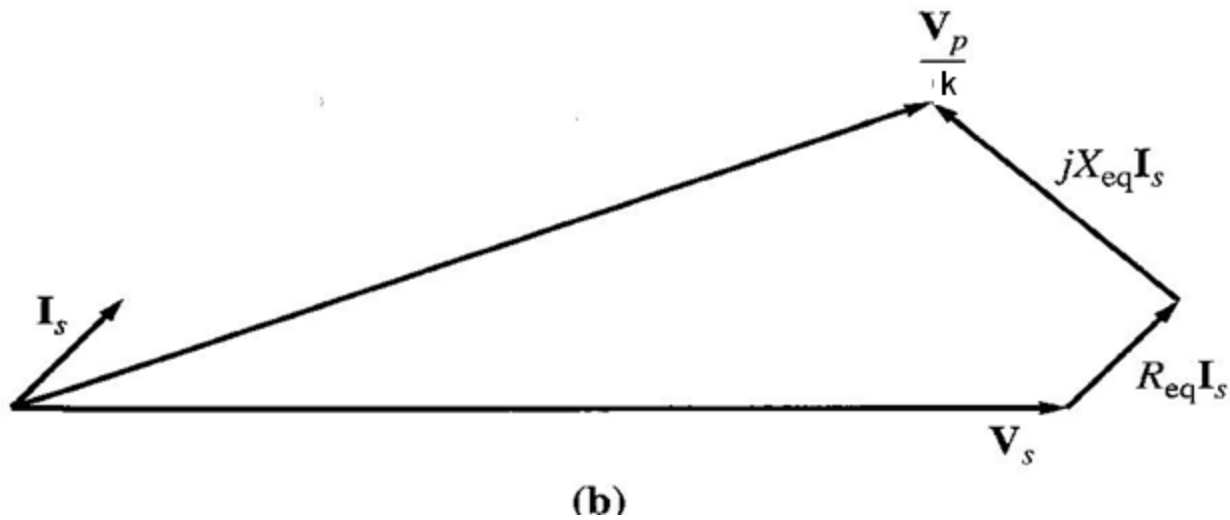With a leading power factor, V_s is higher than the referred V_p so $VR < 0$



Transformer Phasor Diagram

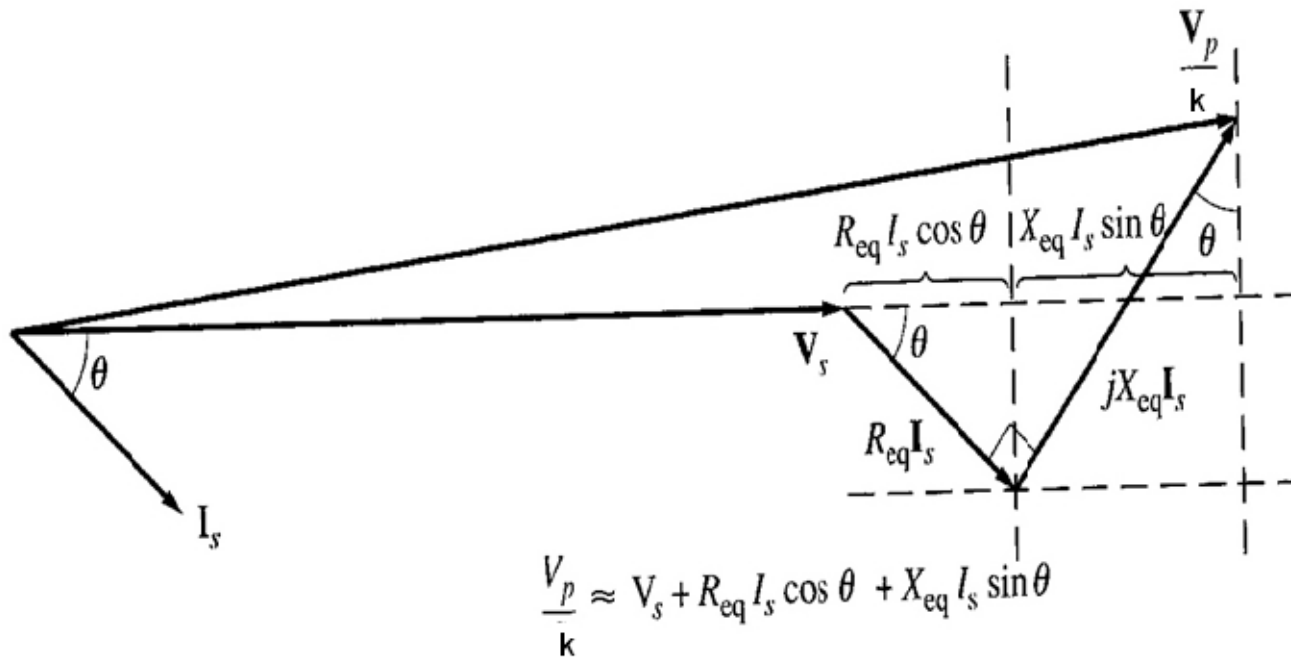For lagging loads, the vertical components of R_{eq} and X_{eq} will partially cancel each other. Due to that, the angle of V_p/a will be very small, hence we can assume that V_p/k is horizontal. Therefore the approximation will be as follows:



Formula: voltage regulation

In terms of secondary values

$$\% \text{ regulation} = \frac{{}_0V_2 - V_2}{{}_0V_2} = \frac{I_2 R_{02} \cos \phi_2 \pm I_2 X_{02} \sin \phi_2}{{}_0V_2}$$

where '+' for lagging and '-' for leading

In terms of primary values

$$\% \text{ regulation} = \frac{V_1 - V_2'}{V_1} = \frac{I_1 R_{01} \cos \phi_1 \pm I_1 X_{01} \sin \phi_1}{V_1}$$

where '+' for lagging and '-' for leading

Transformer Efficiency

Transformer efficiency is defined as (applies to motors, generators and transformers):

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

Copper I^2R losses

Hysteresis losses

Eddy current losses

Therefore, for a transformer, efficiency may be calculated using the following:

$$\eta = \frac{V_S I_S \cos \theta}{P_{Cu} + P_{core} + V_S I_S \cos \theta} \times 100\%$$

Losses in a transformer

Core or Iron loss:

Hysteresis loss $W_h = \eta B_{\max}^{1.6} f V$ watt;

eddy current loss $W_e = \eta B_{\max}^2 f^2 t^2$ watt

Copper loss:

Total Cu loss $= I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} + I_2^2 R_{02}$.

Condition for maximum efficiency

$$\text{Cu loss} = I_1^2 R_{01} \quad \text{or} \quad I_2^2 R_{02} = W_{cu}$$

$$\text{Iron loss} = \text{Hysteresis loss} + \text{Eddy current loss} = W_h + W_e = W_i$$

Considering primary side,

$$\text{Primary input} = V_1 I_1 \cos \phi_1$$

$$\eta = \frac{V_1 I_1 \cos \phi_1 - \text{losses}}{V_1 I_1 \cos \phi_1} = \frac{V_1 I_1 \cos \phi_1 - I_1^2 R_{01} - W_i}{V_1 I_1 \cos \phi_1}$$
$$= 1 - \frac{I_1 R_{01}}{V_1 \cos \phi_1} - \frac{W_i}{V_1 I_1 \cos \phi_1}$$

Differentiating both sides with respect to I_1 , we get

$$\frac{d\eta}{dI_1} = 0 - \frac{R_{01}}{V_1 \cos \phi_1} + \frac{W_i}{V_1 I_1^2 \cos \phi_1}$$

For η to be maximum, $\frac{d\eta}{dI_1} = 0$. Hence, the above equation becomes

$$\frac{R_{01}}{V_1 \cos \phi_1} = \frac{W_i}{V_1 I_1^2 \cos \phi_1} \quad \text{or} \quad W_i = I_1^2 R_{01} \quad \text{or} \quad I_2^2 R_{02}$$

or

$$\text{Cu loss} = \text{Iron loss}$$

Contd.,

The output current corresponding to maximum efficiency is $I_2 = \sqrt{(W_i/R_{02})}$.

The load at which the two losses are equal = Full load $\times \sqrt{\left(\frac{\text{Iron loss}}{\text{F.L. Cu loss}}\right)}$

All day efficiency

$$\text{ordinary commercial efficiency} = \frac{\text{out put in watts}}{\text{input in watts}}$$

$$\eta_{all\ day} = \frac{\text{output in kWh}}{\text{Input in kWh}} \text{ (for 24 hours)}$$

- All day efficiency is always less than the commercial efficiency